
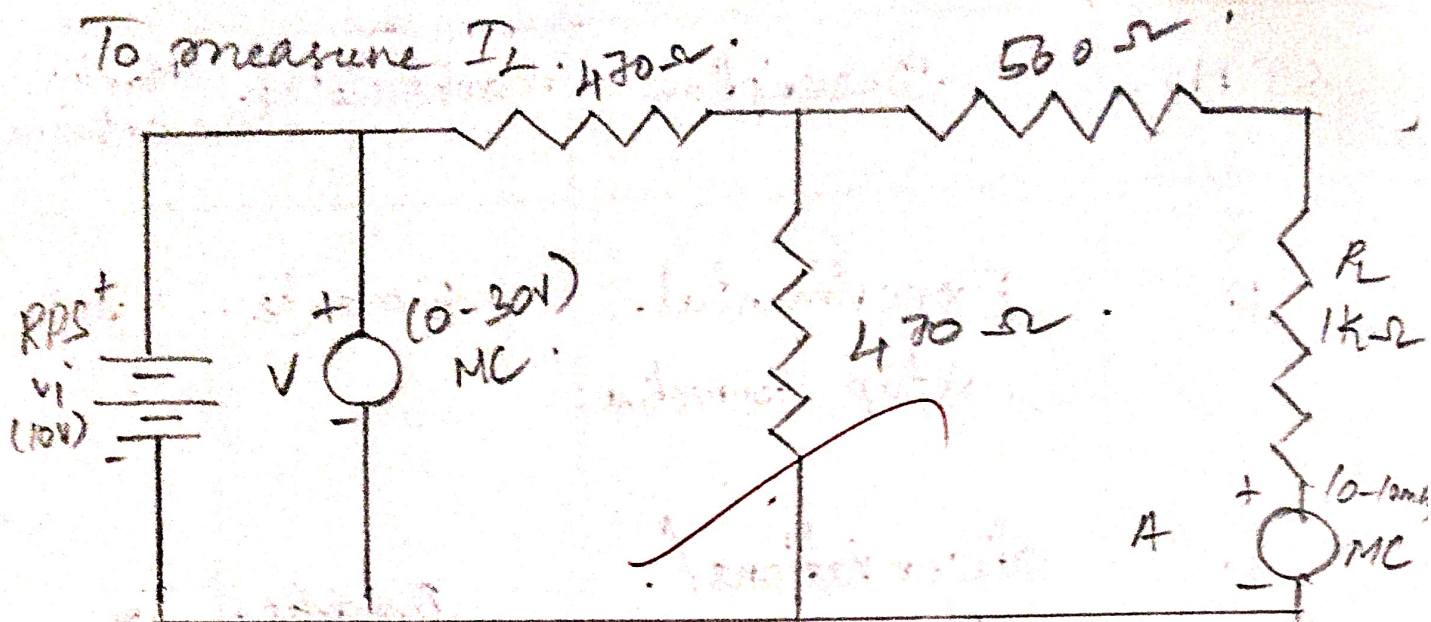


CIRCUIT DIAGRAM: VERIFICATION OF NORTON'S THEOREM.


To measure I_L 470Ω :

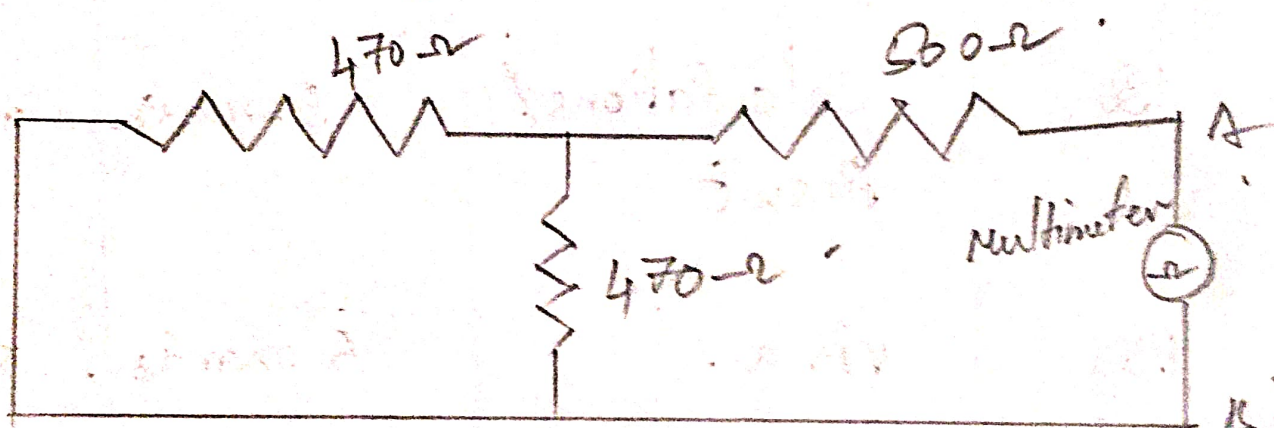

To measure R_{th} or R_N



To measure I_N or I_{sc} :-

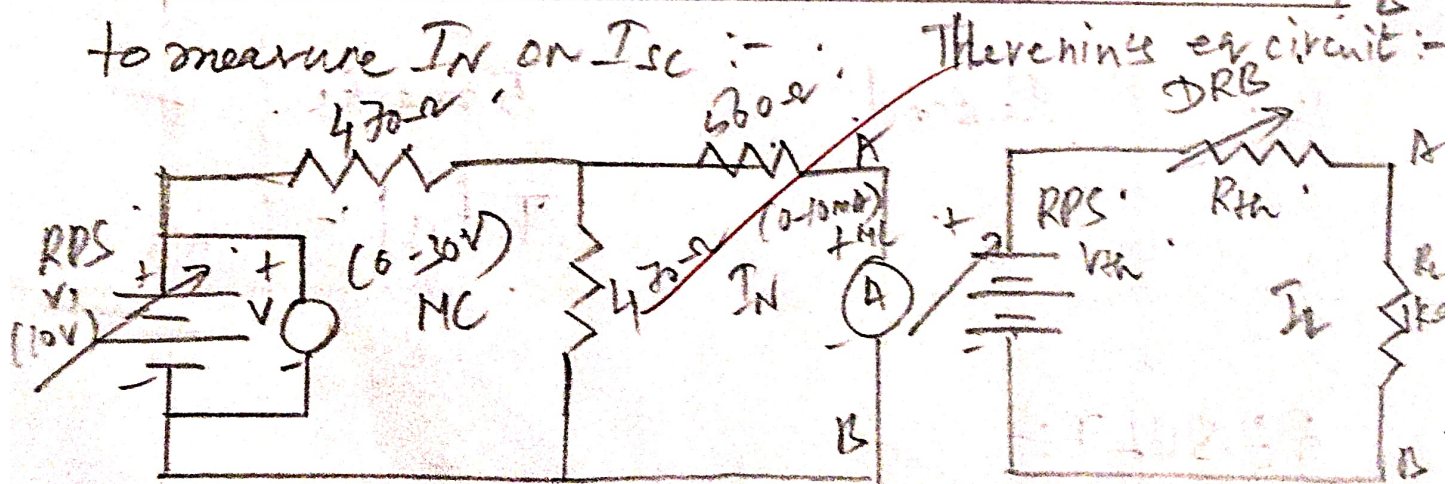

Therewith eq circuit :-

NORTON'S EQUIVALENT CIRCUIT :-

